

# EE4C10 Analog Circuit Design Fundamentals

## Homework Assignment I

Tzong Lin Chua

September 8, 2021

## Contents

Problem 1	1
Problem 2	1
Problem 3	3
Problem 4	7
Problem 5	10
Problem 6	12
Problem 7	13

## Problem 1

For  $I_D = 40\mu A$ :

$$I_D = \frac{1.8V - V_D}{R}$$

$$V_D = 1.8V - I_D R$$

$$V_D = 1.0V$$

Saturation region:

$$V_{GS} = 1.0V > V_{TH}$$

$$V_{GS} - V_{TH} = 0.4V < V_{DS}$$

1.  $\lambda = 0V^{-1}$

$$I_D = \frac{\mu_n C_{OX}}{2} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$L = \frac{\mu_n C_{OX}}{2} \frac{W}{I_D} (V_{GS} - V_{TH})^2$$

$$L = 0.39\mu m$$

2.  $\lambda = 0.06V^{-1}$

$$I_D = \frac{\mu_n C_{OX}}{2} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$L = \frac{\mu_n C_{OX}}{2} \frac{W}{I_D} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$L = 0.41\mu m$$

## Problem 2

1. Bulk of the transistors are connected to the source,  $V_B = V_S$

$$V_{TH} = V_{TH0} + \gamma(\sqrt{|2\varphi_F| + V_{BS}} - \sqrt{|2\varphi_F|})$$

$$V_{TH} = V_{TH0} = 0.33V$$

(a) Transistor M<sub>1</sub>

$$V_{SG} = 2.5V - 1.7V = 0.8V$$

$$I_D = \frac{\mu_p C_{OX}}{2} \frac{W}{L} (V_{SG} - V_{TH})^2$$

$$W = \frac{2LI_D}{\mu_p C_{OX}} \frac{1}{(V_{SG} - V_{TH})^2}$$

$$W_1 = 2.72\mu m$$

(b) Transistor M<sub>2</sub>

$$V_{SG} = 1.7V - 1V = 0.7V$$

$$W = \frac{2LI_D}{\mu_p C_{OX}} \frac{1}{(V_{SG} - V_{TH})^2}$$

$$W_2 = 4.38\mu m$$

(c) Transistor M<sub>3</sub>

$$V_{SG} = 1V$$

$$W = \frac{2LI_D}{\mu_p C_{OX}} \frac{1}{(V_{SG} - V_{TH})^2}$$

$$W_3 = 1.37\mu m$$

2. Bulk terminals are attached to the V<sub>DD</sub>, V<sub>B</sub> = V<sub>DD</sub>.

(a) Transistor M<sub>1</sub>

$$V_{BS} = 2.5V - 2.5V = 0V$$

$$V_{TH} = V_{TH0} + \gamma(\sqrt{|2\varphi_F| + V_{BS}} - \sqrt{|2\varphi_F|})$$

$$V_{TH} = V_{TH0} = 0.33V$$

$$W = \frac{2LI_D}{\mu_p C_{OX}} \frac{1}{(V_{SG} - V_{TH})^2}$$

$$W_1 = 2.72\mu m$$

(b) Transistor M<sub>2</sub>

$$V_{BS} = 2.5V - 1.7V = 0.8V$$

$$V_{TH} = V_{TH0} + \gamma(\sqrt{|2\varphi_F| + V_{BS}} - \sqrt{|2\varphi_F|})$$

$$V_{TH} = V_{TH0} = 0.43V$$

$$W = \frac{2LI_D}{\mu_p C_{OX}} \frac{1}{(V_{SG} - V_{TH})^2}$$

$$W_2 = 8.23\mu m$$

(c) Transistor M<sub>3</sub>

$$V_{BS} = 2.5V - 1.0V = 1.5V$$

$$V_{TH} = V_{TH0} + \gamma(\sqrt{|2\varphi_F| + V_{BS}} - \sqrt{|2\varphi_F|})$$

$$V_{TH} = V_{TH0} = 0.49V$$

$$W = \frac{2LI_D}{\mu_p C_{OX}} \frac{1}{(V_{SG} - V_{TH})^2}$$

$$W_3 = 2.31\mu m$$

## Problem 3

### 1. Testbench and $I_D$ - $V_{GS}$ characteristics of NMOS and PMOS

#### (a) NMOS

##### i. Testbench

```
.lib 'C:\Program Files\LTC\LTspiceXVII\lib\cmp\log018.l' TT  
.dc VGS 0 1.8 0.001
```

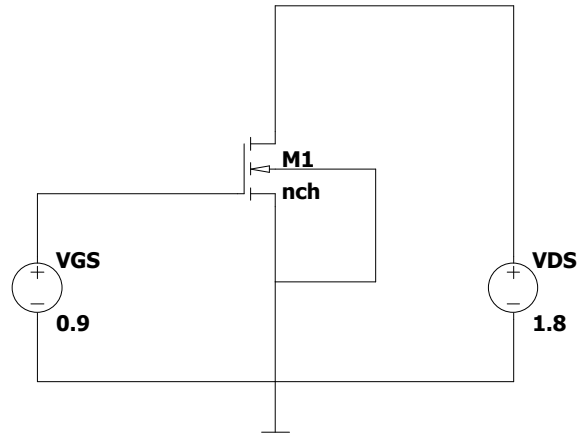


Figure 1: NMOS Testbench

##### ii. $I_D$ - $V_{GS}$

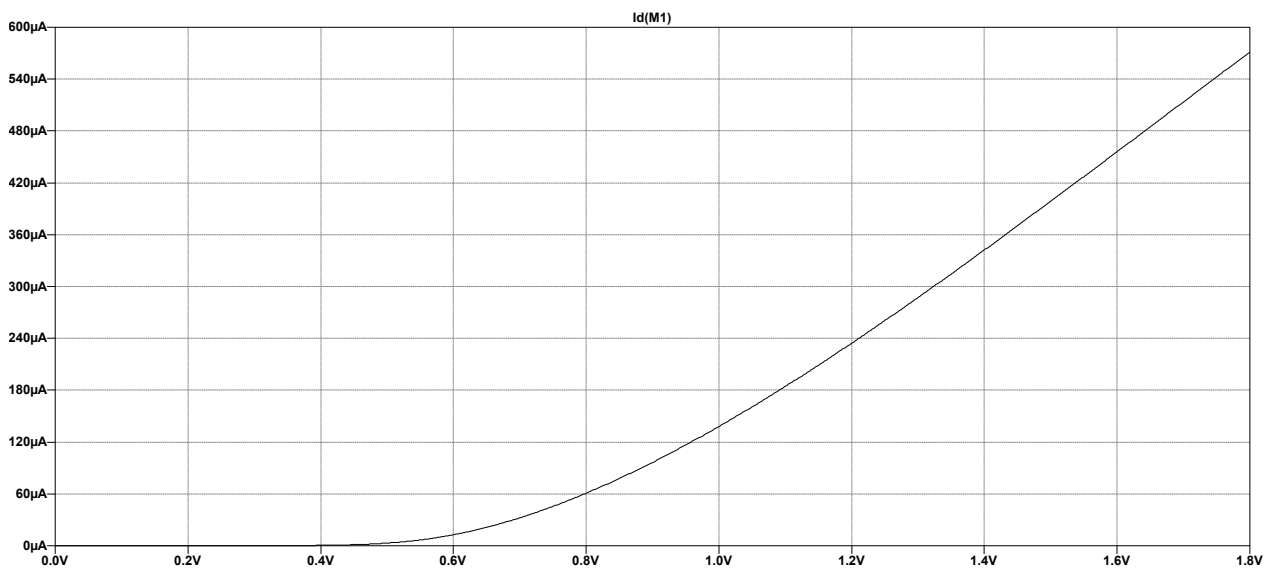


Figure 2: NMOS  $I_D$ - $V_{GS}$

#### (b) PMOS

##### i. Testbench

```
.lib 'C:\Program Files\LTC\LTspiceXVII\lib\cmp\log018.l' TT
.dc VGS -1.8 0 0.001
```

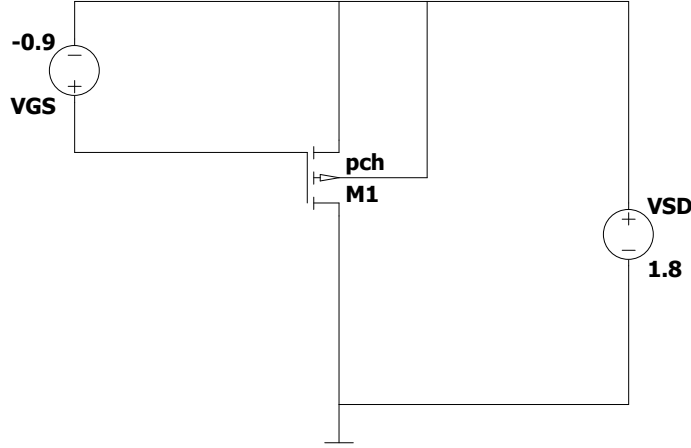


Figure 3: PMOS Testbench

ii.  $I_S$ - $V_{GS}$

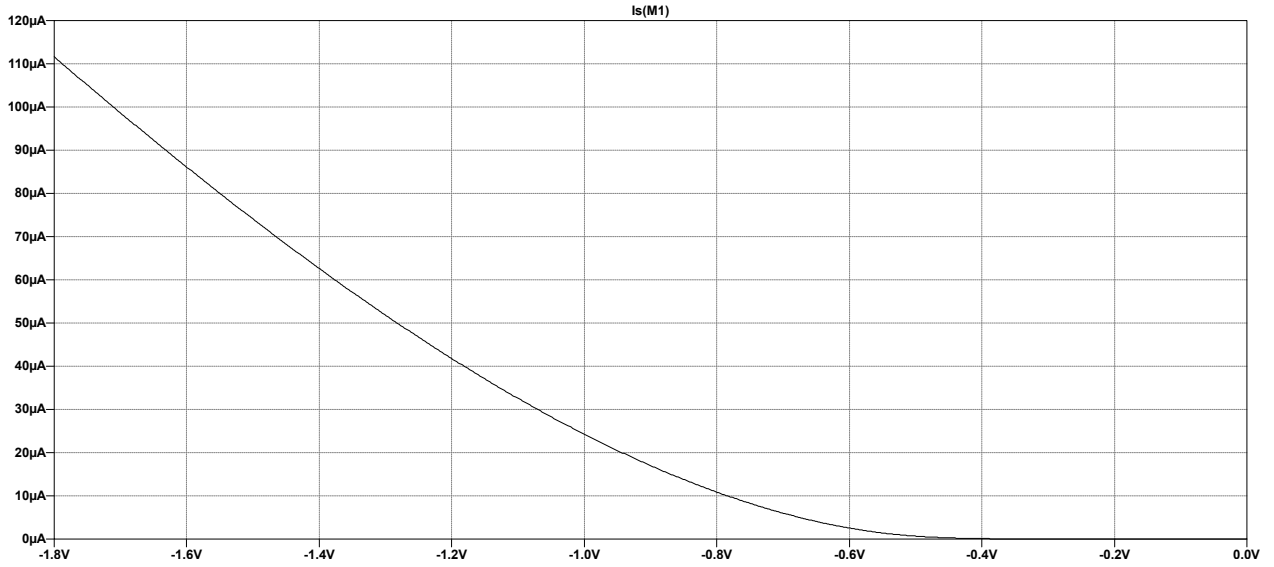


Figure 4: PMOS  $I_S$ - $V_{GS}$

2.  $\mu_{n(p)}C_{OX}$  and  $V_{THn(p)}$

Assuming that channel length modulation is negligible,  $V_{THn}$  for NMOS can be derived from the following relation:

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{THn})^2$$

$$\frac{2I_D}{\mu_n C_{ox}} \frac{L}{W} = (V_{GS} - V_{THn})^2$$

$$\sqrt{\frac{2I_D}{\mu_n C_{ox}} \frac{L}{W}} = V_{GS} - V_{THn}$$

$V_{THn}$  is the x-axis intercept when the saturation region is extrapolated. In the case of PMOS, the relation becomes:

$$\sqrt{\frac{2I_S}{\mu_p C_{ox}} \frac{L}{W}} = V_{SG} + V_{THp}$$

For deriving  $\mu_n C_{OX}$ , since  $V_{THn(p)}$  is constant at specific temperatures. Differentiating both sides with respect to

$V_{GS(SG)}$  will give:

$$\begin{aligned}\frac{d}{dV_{GS}} \sqrt{\frac{2I_D}{\mu_n C_{ox}} \frac{L}{W}} &= \frac{d}{dV_{GS}} (V_{GS} - V_{THn}) \\ \frac{1}{2} \frac{dI_D}{dV_{GS}} \sqrt{\frac{2}{I_D \mu_n C_{ox}} \frac{L}{W}} &= 1 \\ \sqrt{\mu_n C_{ox}} &= \frac{1}{2} \frac{dI_D}{dV_{GS}} \sqrt{\frac{2}{I_D} \frac{L}{W}} \\ \mu_n C_{ox} &= \frac{1}{2} \frac{L}{W} \frac{1}{I_D} \left( \frac{dI_D}{dV_{GS}} \right)^2 \\ \mu_n C_{ox} &= \frac{1}{6I_D} \left( \frac{dI_D}{dV_{GS}} \right)^2\end{aligned}$$

In the case for PMOS, the relation becomes:

$$\mu_p C_{ox} = \frac{1}{6I_S} \left( \frac{dI_S}{dV_{SG}} \right)^2$$

(a) NMOS

i.  $\mu_n C_{OX}$

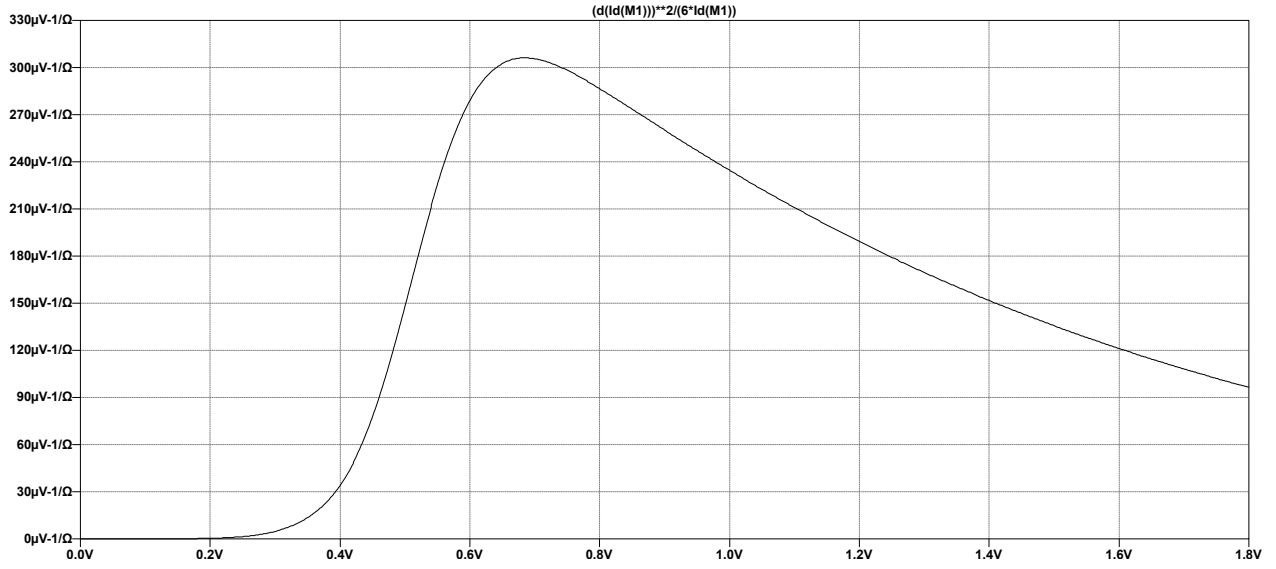


Figure 5: NMOS  $\mu_n C_{OX}$ - $V_{GS}$

ii.  $V_{THn} = 0.44V$

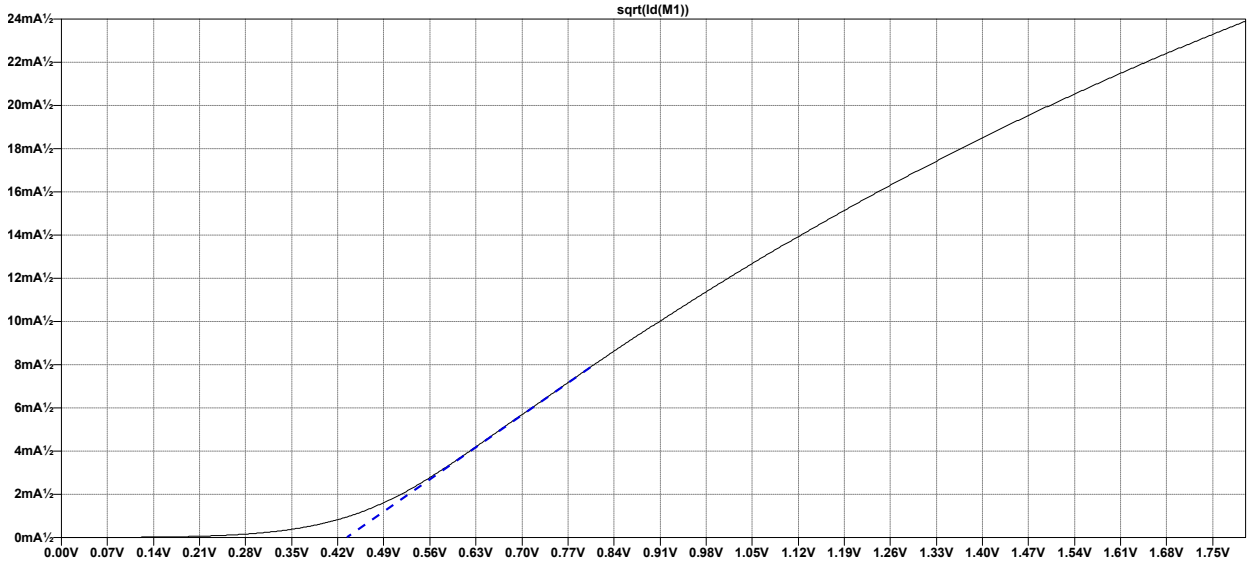


Figure 6: NMOS  $\sqrt{I_D} - V_{GS}$

(b) PMOS

i.  $\mu_p C_{OX}$

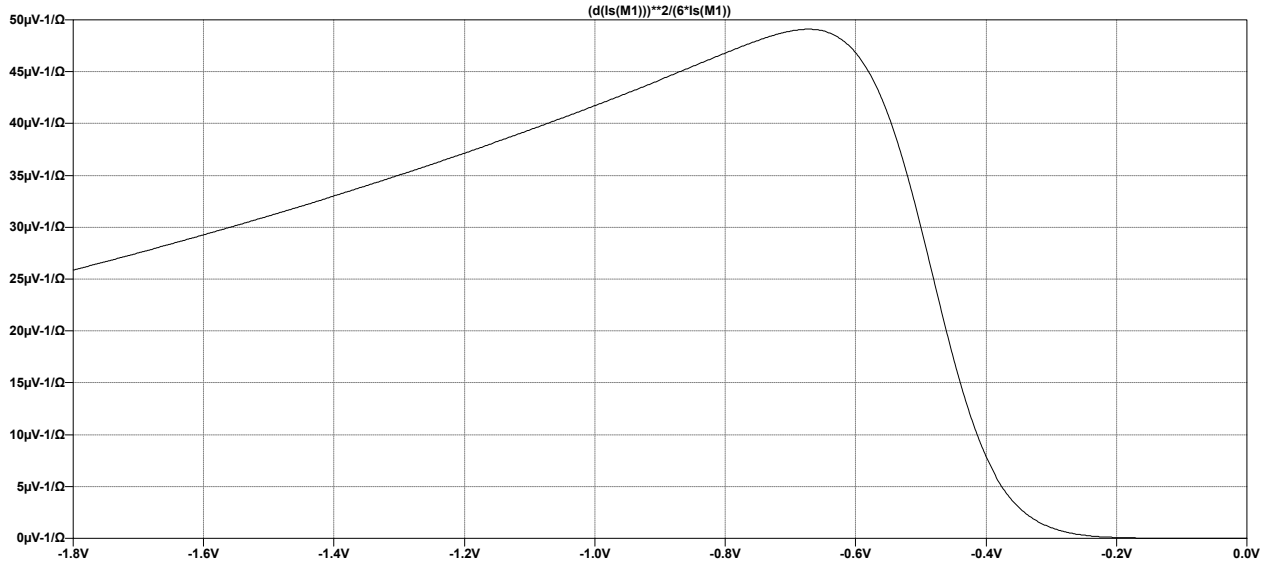


Figure 7: PMOS  $\mu_p C_{OX} - V_{GS}$

ii.  $V_{THp} = -0.42V$

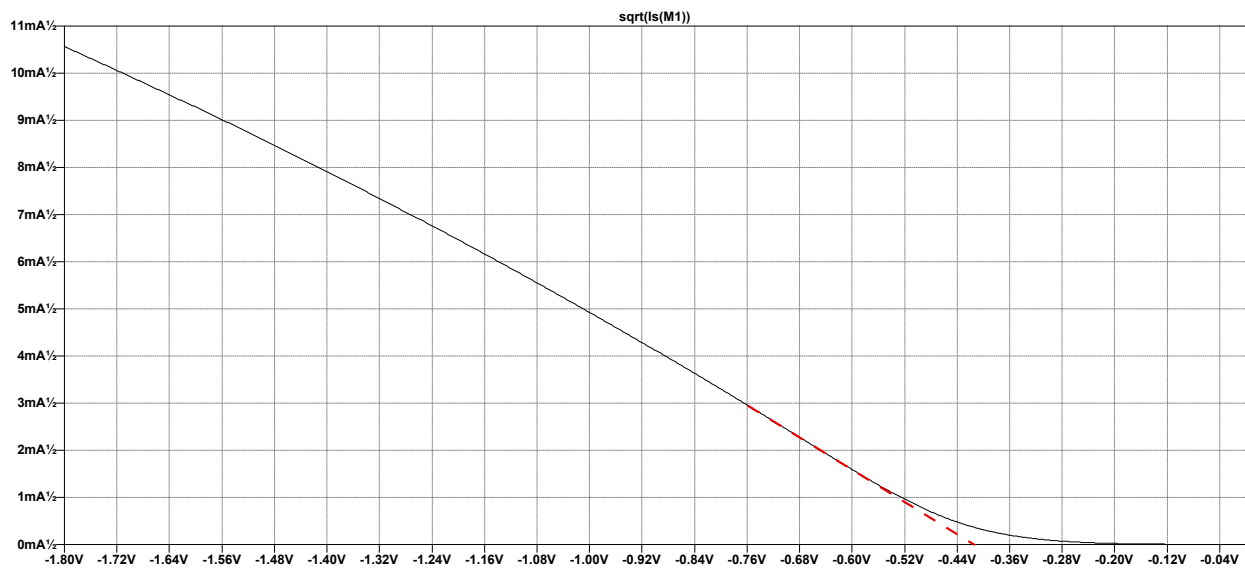


Figure 8: PMOS  $\sqrt{I_S} - V_{GS}$

## Problem 4

1. Testbench and  $I_D$ - $V_{DS}$  characteristics of NMOS and PMOS

(a) NMOS

i. Testbench

```
.lib 'C:\Program Files\LTC\LTspiceXVII\lib\cmp\log018.l' TT
.dc VDS 0 1.8 0.001
```

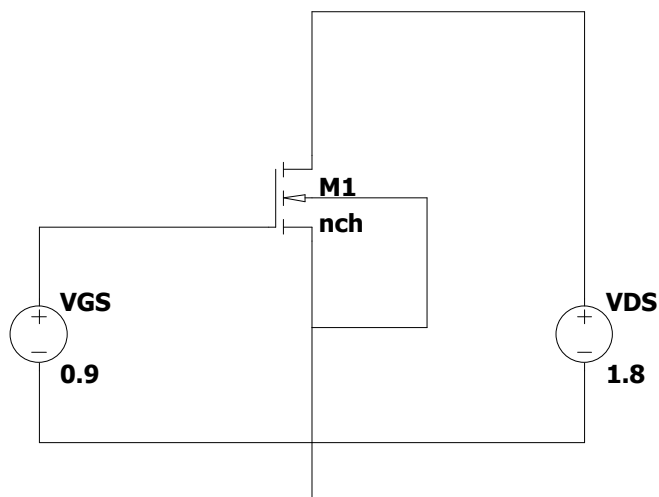


Figure 9: NMOS Testbench

ii.  $I_D$ - $V_{DS}$  characteristics

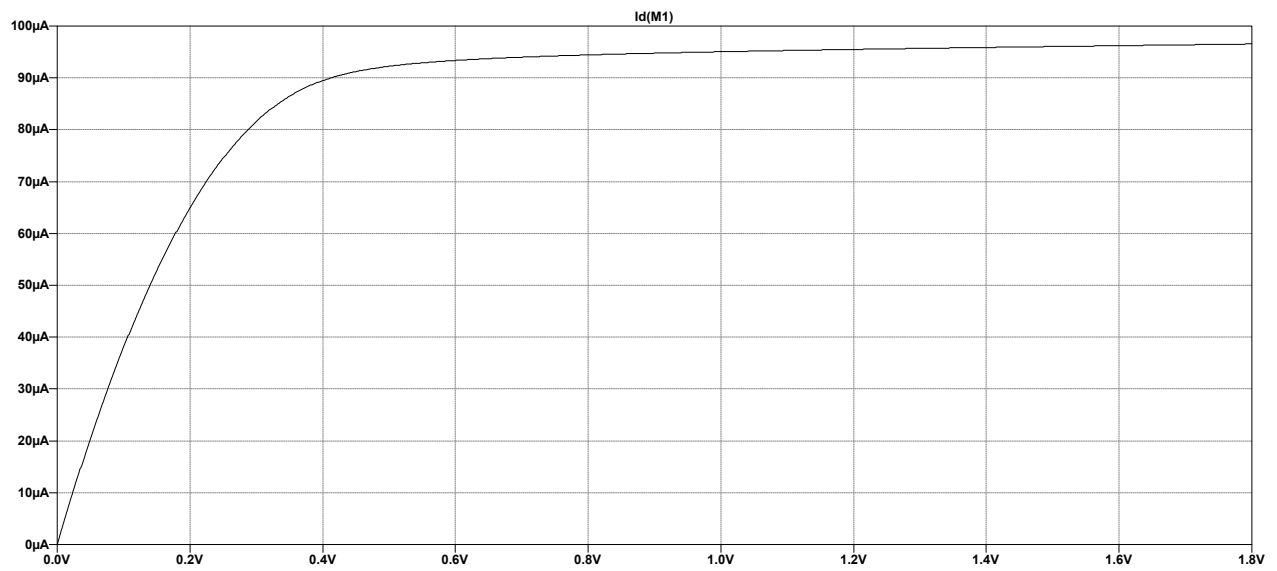


Figure 10: NMOS  $I_D$ - $V_{DS}$

(b) PMOS

i. Testbench

```
.lib 'C:\Program Files\LTC\LTspiceXVII\lib\cmp\log018.l' TT
.dc VDS -1.8 0 0.001
```

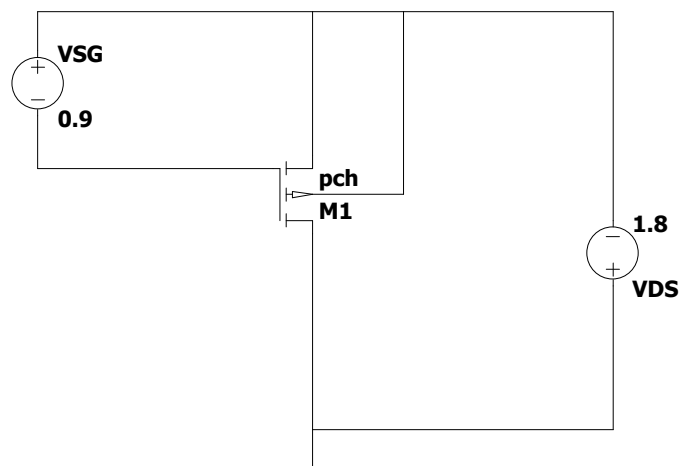


Figure 11: PMOS Testbench

ii.  $I_S$ - $V_{DS}$  characteristics



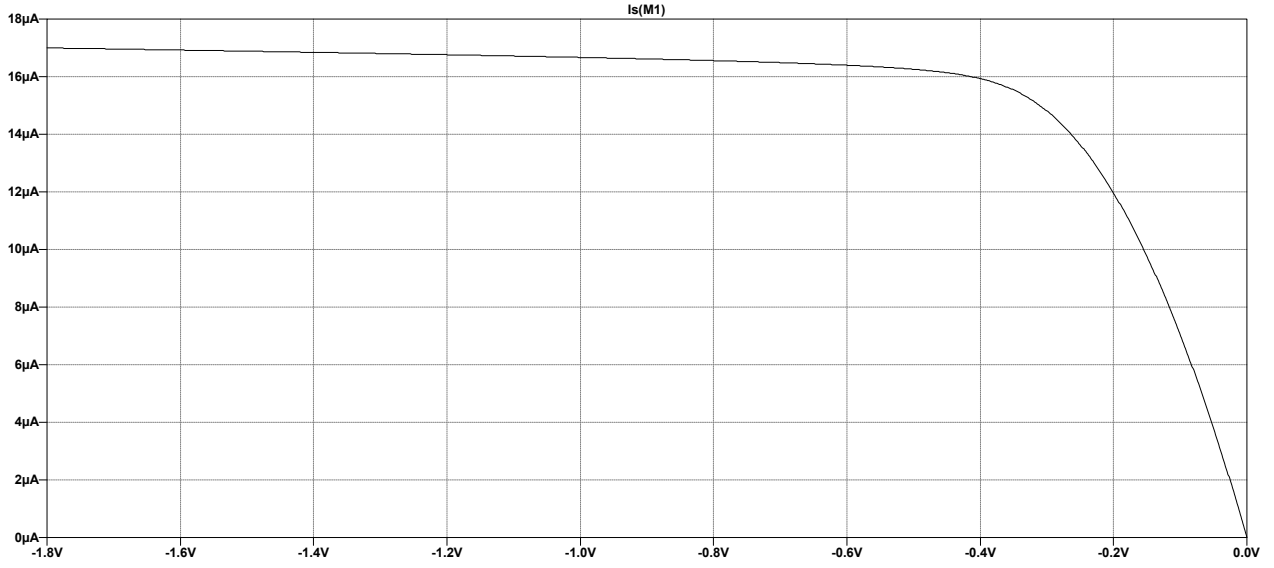


Figure 12: PMOS  $I_S$ - $V_{DS}$

2.  $\lambda_{n(p)}$

Drain current characteristics for NMOS under saturation conditions:

$$I_D = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda_n V_{DS})$$

Differentiating both side with respect to  $V_{DS}$ .

$$\begin{aligned} \frac{dI_D}{dV_{DS}} &= \frac{d}{dV_{DS}} \left( \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda_n V_{DS}) \right) \\ \frac{dI_D}{dV_{DS}} &= \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{TH})^2 \lambda_n \end{aligned}$$

Assuming that the body-effect is small:

$$I_D \approx \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$\begin{aligned} \frac{dI_D}{dV_{DS}} &\approx I_D \lambda_n \\ \lambda_n &\approx \frac{1}{I_D} \frac{dI_D}{dV_{DS}} \end{aligned}$$

In the case of PMOS:

$$\lambda_p \approx \frac{1}{I_S} \frac{dI_S}{dV_{SD}}$$

(a)  $\lambda_n = 0.18V^{-1}$

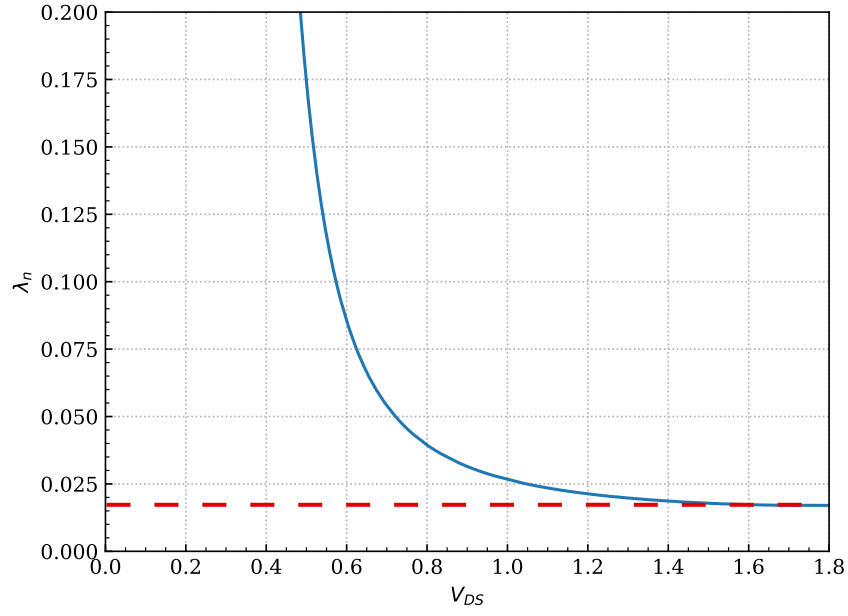


Figure 13: NMOS  $\lambda_n - V_{DS}$

(b)  $\lambda_p = -0.022V^{-1}$

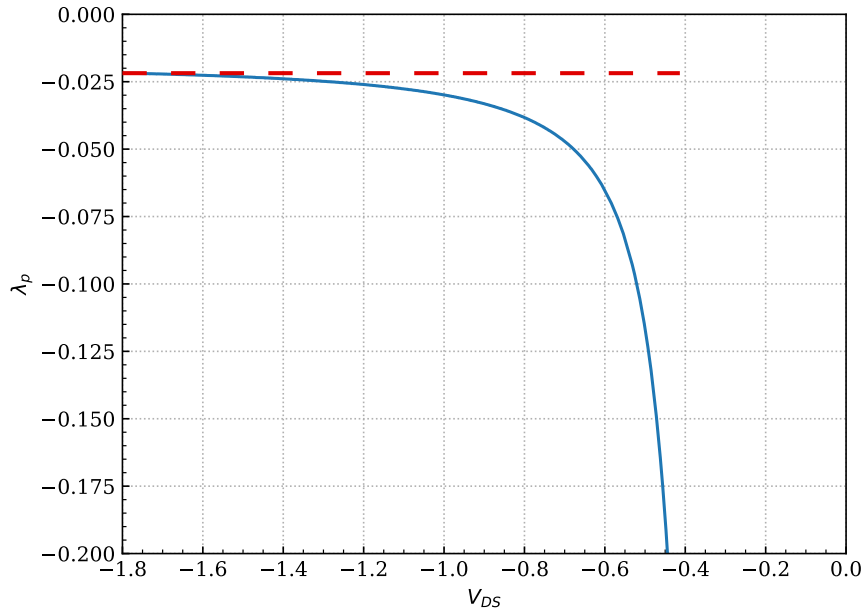


Figure 14: PMOS  $\lambda_p - V_{DS}$

## Problem 5

$g_m$  for NMOS is approximately:

$$g_m \approx \frac{\partial I_D}{\partial V_{GS}}$$

For PMOS:

$$g_m \approx \frac{\partial I_S}{\partial V_{SG}}$$

1.  $\frac{g_m}{I_D} - V_{GS}$

(a) NMOS

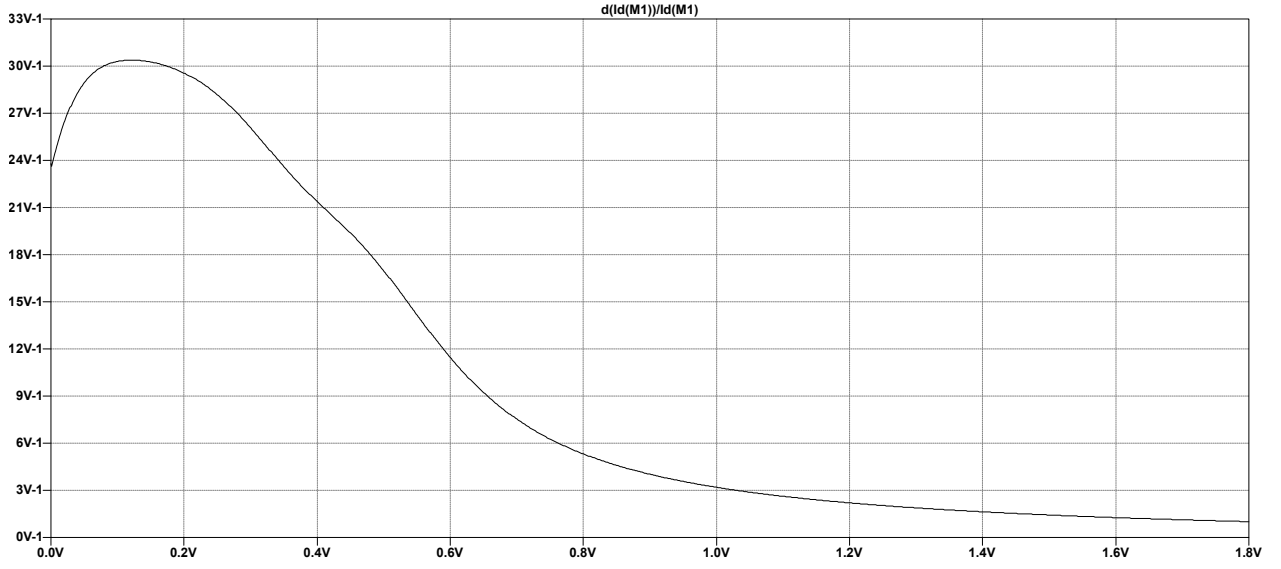


Figure 15: NMOS  $\frac{g_m}{I_D} - V_{GS}$

(b) PMOS

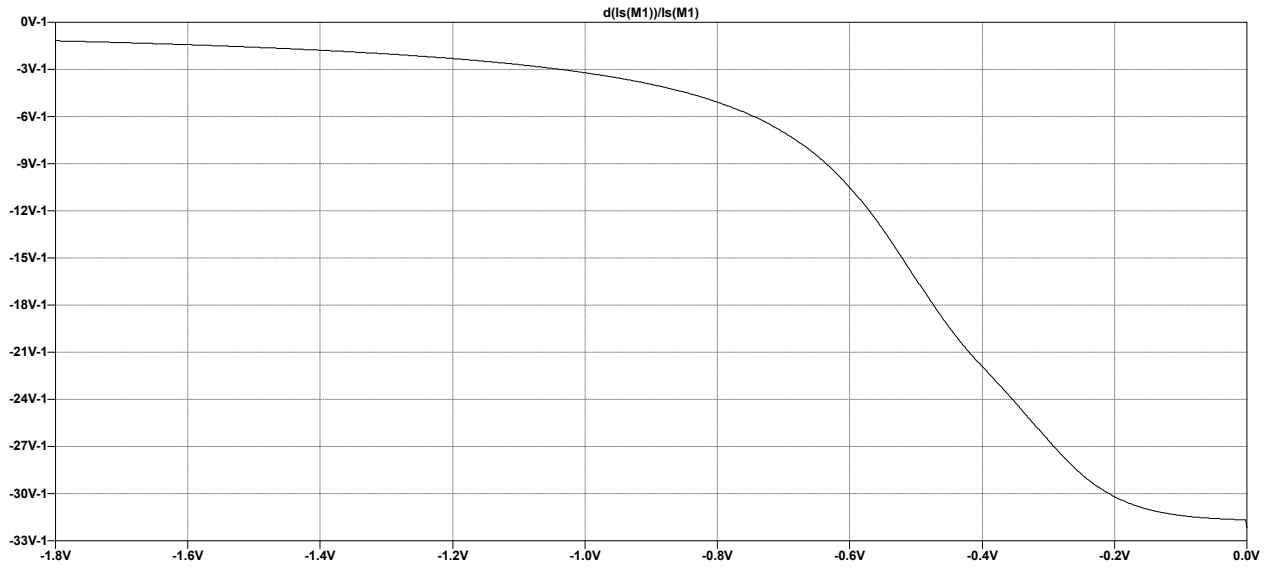


Figure 16: PMOS  $\frac{g_m}{I_S} - V_{GS}$

2.  $\max(|\frac{g_m}{I_{D(S)}}|)$

(a) NMOS

$$\max(|\frac{g_m}{I_D}|) = 30.4V^{-1}$$

(b) PMOS

$$\max(|\frac{g_m}{I_S}|) = 31.7V^{-1}$$

3. Slope factor, n

(a) NMOS

$$\max(|\frac{g_m}{I_D}|) = 30.4V^{-1}$$

$$\frac{1}{nV_t} = 30.4V^{-1}$$

$$n = \frac{1}{0.026 \times 30.4}$$

$$n = 1.27$$

(b) PMOS

$$\max(|\frac{g_m}{I_S}|) = 31.7V^{-1}$$

$$\frac{1}{nV_t} = 31.7V^{-1}$$

$$n = \frac{1}{0.026 \times 31.7}$$

$$n = 1.21$$

## Problem 6

1. Small-signal Model

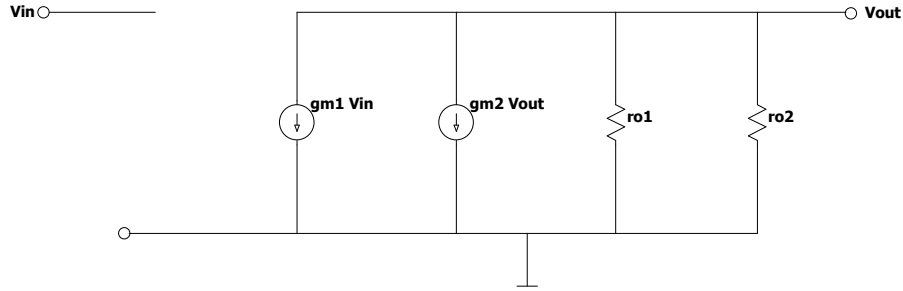


Figure 17: Small signal model

2.  $\lambda = 0V^{-1}$

(a)  $A_V = \frac{v_{out}}{v_{in}}$

$$(g_{m1}v_{in} + g_{m2}v_{out}) = 0$$

$$A_V = \frac{v_{out}}{v_{in}} = -\frac{g_{m1}}{g_{m2}}$$

(b)  $R_{out}$

$$R_{out} = \frac{1}{g_{m2}}$$

3.  $\lambda \neq 0V^{-1}$

(a)  $A_V = \frac{v_{out}}{v_{in}}$

$$-v_{out} = (g_{m1}v_{in} + g_{m2}v_{out})(r_{o1}/r_{o2})$$

$$-v_{in}g_{m1}(r_{o1}/r_{o2}) = (1 + g_{m2}(r_{o1}/r_{o2}))v_{out}$$

$$A_V = \frac{v_{out}}{v_{in}} = -\frac{g_{m1}}{g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}}$$

(b)  $R_{out}$

$$R_{out} = \frac{1}{g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}}$$

## Problem 7

1.  $V_{out}$ - $V_{in}$  relation when:

(a)  $M_1$  and  $M_2$  under subthreshold conditions

$$V_{TH_n} = 0.44V$$

$$V_{TH_p} = -0.42V$$

$$\mu_n C_{OX_n} = 306 \mu A V^{-2}$$

$$\mu_p C_{OX_p} = 49 \mu A V^{-2}$$

$$n_n = 1.27$$

$$n_p = 1.21$$

$$I_{D_1} = I_{D_2}$$

$$(\mu_n C_{OX_n} (n-1) \frac{W_n}{L_n} V_T^2) e^{\frac{V_{in} - V_{TH_n}}{n_n V_T}} = (\mu_p C_{OX_p} (n-1) \frac{W_p}{L_p} V_T^2) e^{\frac{V_{DD} - V_{out} + V_{TH_p}}{n_p V_T}}$$

$$247 e^{\frac{V_{in} - 0.44}{0.033}} = 154 e^{\frac{1.8 - V_{out} - 0.42}{0.031}}$$

$$\ln(1.6) + \frac{V_{in} - 0.44}{0.033} = \frac{1.38 - V_{out}}{0.031}$$

$$0.015 + V_{in} - 0.44 \approx 1.38 - V_{out}$$

$$V_{out} \approx 1.8V - V_{in}$$

$$V_{in} < 0.44V$$

(b)  $M_1$  and  $M_2$  at saturation

$$I_{D_1} = I_{D_2}$$

$$\frac{\mu_n C_{OX_n}}{2} \frac{W_n}{L_n} (V_{GS_1} - V_{TH_n})^2 = \frac{\mu_p C_{OX_p}}{2} \frac{W_p}{L_p} (V_{SG_2} + V_{TH_p})^2$$

$$918(V_{in} - 0.44)^2 = 735(1.8 - V_{out} - 0.42)^2$$

$$1.12(V_{in} - 0.44) = 1.38 - V_{out}$$

$$V_{out} = 1.87V - 1.12V_{in}$$

Saturation conditions for  $M_1$ :

$$V_{GS_1} - V_{TH_1} < V_{DS}$$

$$V_{in} - 0.44V < V_{out}$$

$$V_{in} - 0.44V < 1.87V - 1.12V_{in}$$

$$2.12V_{in} < 2.31V$$

$$V_{in} < 1.09V$$

Condition for  $M_1$  and  $M_2$  at saturation:

$$0.44V < V_{in} < 1.09V$$

(c)  $M_1$  at triode and  $M_2$  at saturation

$$I_{D_1} = I_{D_2}$$

$$\mu_n C_{OX_n} \frac{W_n}{L_n} [(V_{GS_1} - V_{TH_n})V_{DS} - \frac{V_{DS}^2}{2}] = \frac{\mu_p C_{OX_p}}{2} \frac{W_p}{L_p} (V_{SG_2} + V_{TH_p})^2$$

$$2.50[(V_{in} - 0.44V)V_{out} - \frac{V_{out}^2}{2}] = (V_{DD} - V_{out} - 0.42V)^2$$

$$V_{out} = \frac{(2.5V_{in} + 1.66) - \sqrt{(2.5V_{in} + 1.66)^2 - 17.1}}{4.5}$$

Condition:

$$V_{in} > 1.09V$$

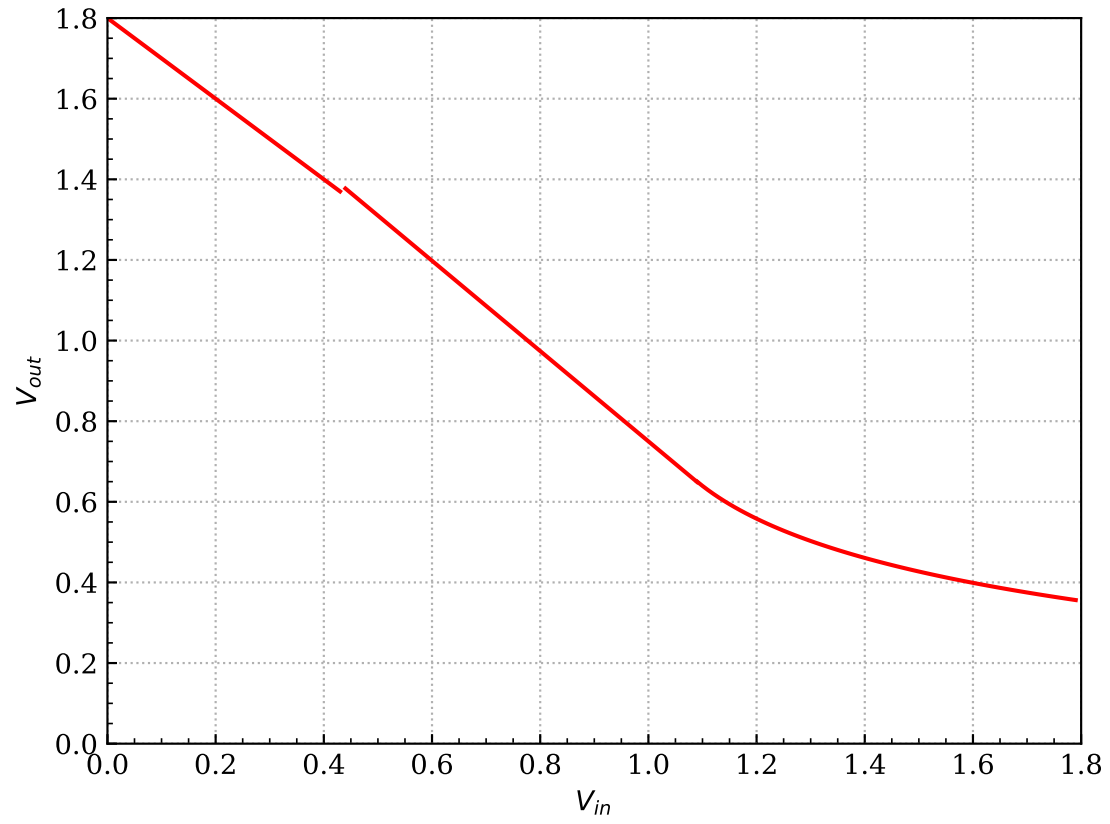


Figure 18: Calculated  $V_{out} - V_{in}$

## 2. Simulated $V_{out}$ - $V_{in}$ relation using LTSpice

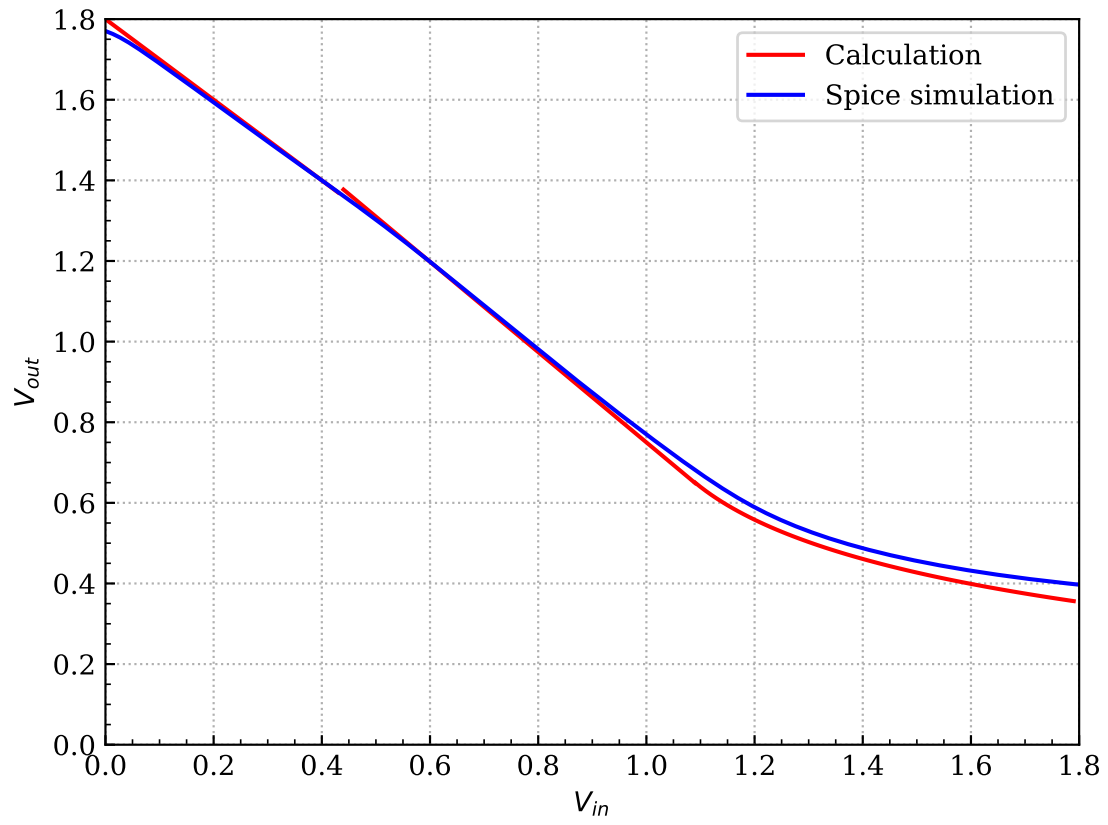


Figure 19: Simulated and calculated  $V_{out} - V_{in}$

3. Maximum small-signal gain For maximum small-signal gain:

$$\max(|A_V|) = \max\left(\left|\frac{\partial V_{out}}{\partial V_{in}}\right|\right)$$

$$V_{in} \approx 0.69V$$

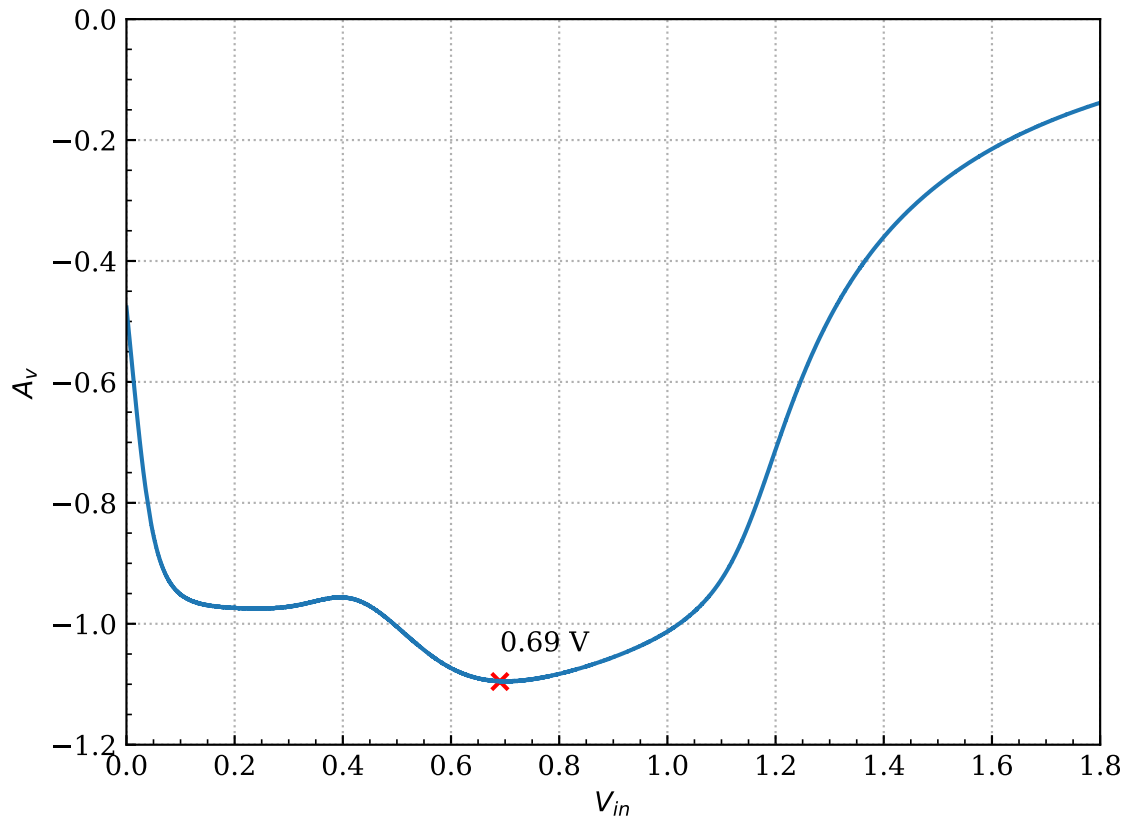


Figure 20:  $A_v - V_{in}$

4. Small signal parameters:

(a)  $|A_v| = 787.83 \text{ m dB} = 1.09$

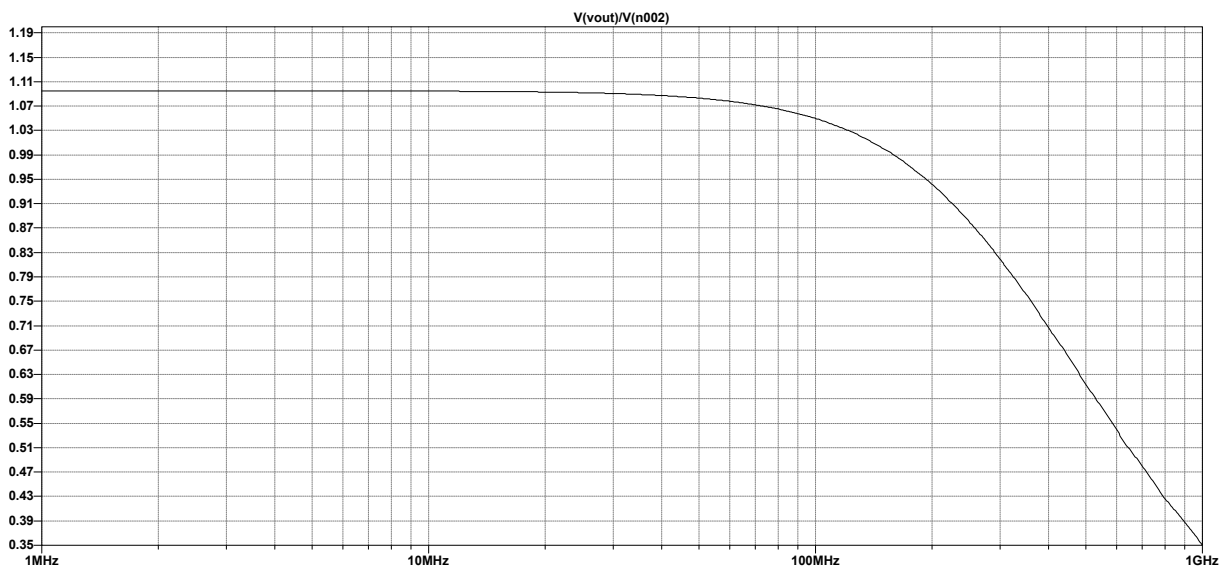


Figure 21:  $A_v$  at  $V_{in} = 0.69 \text{ V}$

(b)  $R_{out} = 4.73 \text{ k}\Omega$



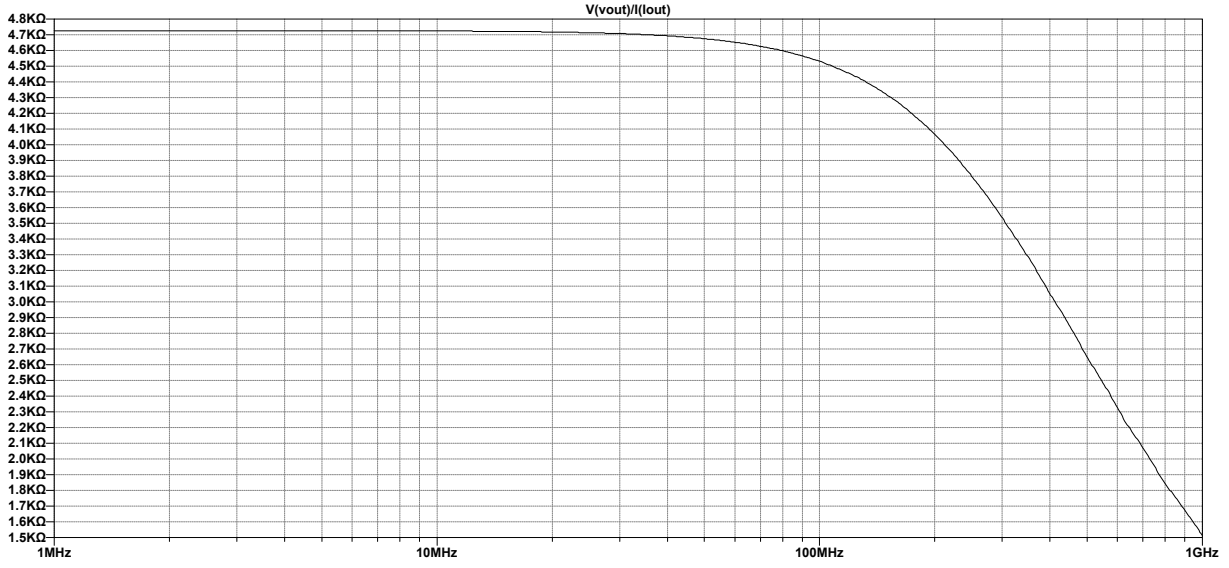


Figure 22:  $R_{out}$  at  $V_{in} = 0.69V$

5.  $g_m$  and  $g_{ds}$  From 7(d),

$$A_V = 1.09$$

$$R_{out} = 4.73k\Omega$$

From 6(c),

$$g_{m_1} = 2.32e-04\Omega^{-1}$$

$$g_{m_2} = 2.09e-04\Omega^{-1}$$

$$g_{DS_1} = \frac{1}{r_{o_1}} = 8.66e-07\Omega^{-1}$$

$$g_{DS_2} = \frac{1}{r_{o_2}} = 1.28e-06\Omega^{-1}$$

$$A_V = \frac{v_{out}}{v_{in}} = -\frac{g_{m1}}{g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}}$$

$$\approx 1.10$$

$$R_{out} = \frac{1}{g_{m2} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}}$$

$$R_{out} = 4.74k\Omega$$