

# Homework Assignment I

Start date: 30/08/2021

Due date: 10/09/2021

Please upload your homework via Brightspace

## FORMULARY

$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) \quad (1)$$

$$I_D = \mu C_{ox} \frac{W}{L} \left[ (V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right] \quad (2)$$

$$V_{TH} = V_{TH0} + \gamma \left( \sqrt{2\phi_F + V_{SB}} - \sqrt{|2\phi_F|} \right) \quad (3)$$

$$I_D = I_0 e^{\frac{V_{GS}}{nV_T}} \quad (4)$$


$$\text{Long Channel : } I_0 = \mu C_{ox} (n-1) \frac{W}{L} V_T^2 \quad (5)$$

$$\text{Slope factor: } n = 1 + \frac{C_d}{C_{ox}} \quad (6)$$

## INSTRUCTIONS

1. Solutions must be submitted in PDF file named "Name\_Surname\_HW1.pdf". Descriptions of the simulation and simulation results must be included in the PDF file, while schematics used for simulations must be compressed in a single ZIP file named "Name\_Surname\_HW1.zip" containing the Itspice files. Converted photographs are not accepted. Please avoid hand-written reports and graphs. Simulation waveforms should have a white background.
2. Late submissions would not be accepted.
3. For the simulation's questions, attach a Itspice file used for each question that must be directly simulatable.

 1. **(1 point)** The NMOS transistor in the circuit of Fig. 1 has  $V_{TH} = 0.6$  V,  $\mu_n C_{ox} = 130$   $\mu\text{A}/\text{V}^2$  and  $W = 1.5$   $\mu\text{m}$ . Find the values required for  $L$  and  $V_D$  in order to establish a drain current of 40  $\mu\text{A}$  for  $R = 20\text{k}\Omega$  for
  - a)  $\lambda = 0$   $\text{V}^{-1}$
  - b)  $\lambda = 0.06$   $\text{V}^{-1}$ .



2. **(1 point)** The PMOS transistors in the circuit of Fig. 2 have  $V_{TH0} = 0.33$  V,  $\mu_p C_{ox} = 120$   $\mu\text{A}/\text{V}^2$ ,  $\lambda = 0$   $\text{V}^{-1}$ , and  $L_1 = L_2 = L_3 = 0.40$   $\mu\text{m}$ .
  - a) Considering that the bulk of the transistors are connected to the source, find the required values of gate width for each of  $M_1$ ,  $M_2$ , and  $M_3$  to obtain the voltage and current values indicated.
  - b) Now, consider that the bulk terminals are attached to the  $V_{DD}$  and that  $\gamma = 0.25$   $\text{V}^{1/2}$  and  $\phi_F = 0.35$  V and calculate the new gate widths.

 


Figure 2.

The parameters of the quadratic and sub-threshold conduction models can be extracted from the BSIM model through SPICE simulation. Use  $V_{DD} = 1.8$  V and  $W = 3$   $\mu\text{m}/L = 1$   $\mu\text{m}$  for the NMOS and PMOS transistors in questions from 3 to 6 and using LTSpice do the following:

**[TIP: use the mathematic functions of the LTSPICE or MATLAB to process the data.]**

3. **(1.5 points)**
  - a) Build a test bench and trace the  $I_D$ - $V_{GS}$  characteristic (set the body-source potential difference to 0 V) for the pmos and nmos transistors.
  - b) Derive the parameters  $\mu_{n(p)} C_{ox}$  and  $V_{THn(p)}$  from this curve.
4. **(1 point)**
  - a) Build a test bench and trace the  $I_D$ - $V_{DS}$  for characteristic for  $V_{GSn} = 0.9$  V and  $V_{SGp} = 0.9$  V (set the body-source potential difference to 0 V).
  - b) Derive the parameter  $\lambda_{n(p)}$  from this curve.
5. **(1 point)**
  - a) Plot  $g_m/I_D$  versus  $V_{GS}$  for both NMOS and PMOS
  - b) Based on this information, get the maximum  $g_m/I_D$  of the technology at room temperature
  - c) Derive the slope factor  $n$ .

6. (1.5 points) Consider Fig. 4 and that transistor  $M_1$  is operating in saturation,
- draw the low-frequency (i.e., without capacitances) small-signal model of the circuit considering non-zero  $\lambda$
  - calculate the expression for the relation  $A_v = V_{out}/V_{in}$  and the output impedance  $R_{OUT}$  seen by the terminal  $V_{OUT}$  considering  $\lambda=0$
  - same as 6b), but now with non-zero  $\lambda$ .

 


Figure 4.

7. (3 points) Consider the parameters extracted in exercises 3,4 and 5 with the circuit of Fig. 4 with the following sizing:  $L_1 = 1 \mu\text{m}$ ,  $W_1 = 3 \mu\text{m}$ ,  $L_2 = 1 \mu\text{m}$  and  $W_2 = 15 \mu\text{m}$  and with  $V_{DD} = 1.8 \text{ V}$  and  $\lambda_{n(p)} = 0$ , do the following:  
(If you were not able to do 3,4 and 5 use:  $\mu_n C_{ox} = 500 \mu\text{A}/\text{V}^2$ ,  $\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$ ,  $V_{THn} = 0.42\text{V}$ ,  $V_{THp} = -0.43\text{V}$ ,  $n = 1.1$ )
- Calculate and plot  $V_{out}$  versus  $V_{in}$  for  $V_{in}$  from 0 V to 1.8 V using the simplified models for strong and weak inversion levels in the correct regions.
  - Use LTSpice to plot  $V_{out}$  versus  $V_{in}$  for  $V_{in}$  from 0 V to 1.8 V and plot it together with the calculated expression on the 7a),
  - Derive the small-signal gain  $A_v = V_{out}/V_{in}$ , and find out the bias point for  $V_{GS1}$  for the maximum voltage gain.
  - Trace the small-signal model parameters  $A_v$  and  $R_{out}$  using AC sweep from 1MHz to 1GHz with the  $V_{GS1}$  bias point obtained in 7b).
  - Using the setup in 7d) run both .ac and .op simultaneously in LTSpice (see figure 5) and view the View→SPICE Error Log (see figure 6). Use Gm and Gds in the Spice Error Log in the found equations from 6c) and compare them with the results from 7d).

```
.ac dec 10 1Meg 1G
.op
```

Figure 5.

SPICE Error Log

Figure 6.

---- END OF THE ASSIGNMENT ----