

EE4C10 Analog Circuit Design Fundamentals

Homework Assignment IV

Tzong Lin Chua

October 7, 2021

Contents

Simulation Files	1
Problem 1	1
Problem 2	2
Problem 3	3
Problem 4	5

Simulation Files

Each question with simulation files will have their respective subfolder.

Running the simulation files should be able to directly plot the graphs used (configured in the *.plt file). The folders for each question are arranged as follows after extracting:

spice
q3
a
b
c
d
q4
a
b
c

Problem 1

(a) DC gain, $|\frac{V_{out}}{V_{in}}|$

KCL at drain node,

$$\frac{V_{out}}{R_D} = (g_m + g_{mb})v_s$$
$$\frac{V_{out}}{v_s} = (g_m + g_{mb})R_D$$

KCL at source node,

$$\frac{V_{in} - V_S}{R_S} = (g_m + g_{mb})v_s$$
$$\frac{V_{in}}{v_s} = R_S(g_m + g_{mb}) + 1$$

DC gain,

$$|\frac{V_{out}}{V_{in}}| = \frac{(g_m + g_{mb})R_D}{(g_m + g_{mb})R_S + 1}$$

(b) Pole of output node, $\omega_{p,out}$

$$R_{out} = R_D$$

$$C_{out} = C_{DB} + C_{GD}$$

$$\omega_{p,out} = \frac{1}{R_D(C_{DB} + C_{GD})}$$

(c) Input impedance,

$$Z_{IN} = \frac{1}{g_m + g_{mb} + s(C_{GS} + C_{SB})}$$

(d) Source capacitance, C_S , and input pole, $\omega_{p,in}$,

$$C_S = C_{GS} + C_{SB}$$

$$\omega_{p,in} = \frac{g_m + g_{mb} + R_S^{-1}}{C_S}$$

$$= \frac{g_m + g_{mb} + R_S^{-1}}{C_{GS} + C_{SB}}$$

Problem 2

(a) Transfer function, $\frac{V_{out}(s)}{V_{in}(s)}$,

DC gain,

$$\left| \frac{V_{out}(S)}{V_{in}(s)} \right| = 1$$

Poles at gate and source nodes,

$$\omega_{p,G} = \frac{1}{R_S(C_{GB} + C_{GD})}$$

$$\omega_{p,D} = \frac{g_m}{C_{SB}}$$

Transfer function,

$$\frac{V_{out}(S)}{V_{in}(s)} = \frac{1}{1 + sR_S(C_{GB} + C_{GD})} \frac{1}{1 + s\frac{C_{SB}}{g_m}}$$

$$= \frac{1}{(1 + sR_S(C_{GB} + C_{GD}))(1 + \frac{sC_{SB}}{g_m})}$$

(b) Poles at gate and source nodes,

$$\omega_{p,G} = \frac{1}{R_S(C_{GB} + C_{GD})}$$

$$\omega_{p,D} = \frac{g_m}{C_{SB}}$$

(c) Input impedance,

$$Z_{in} = \frac{1}{s(C_{GB} + C_{GD})}$$

Problem 3

(a) Testbench,

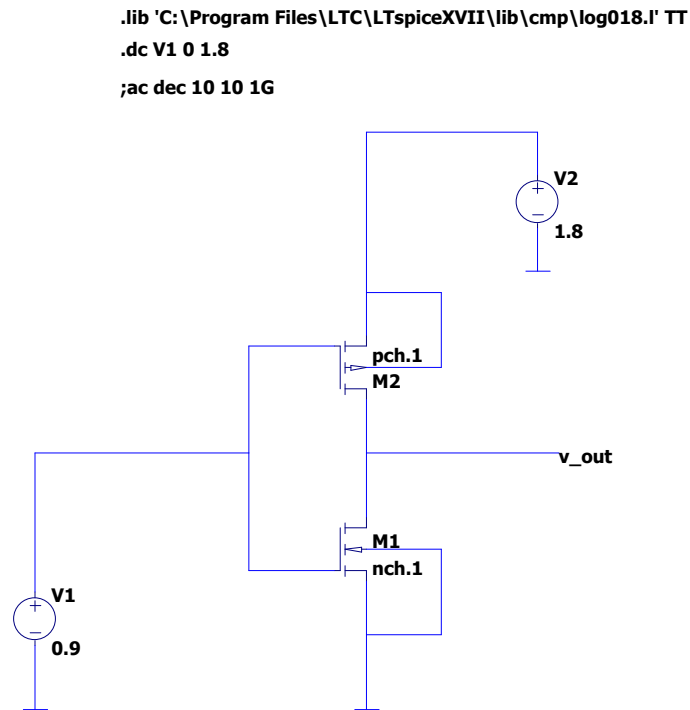


Figure 1: Inverter testbench

DC transfer curve,

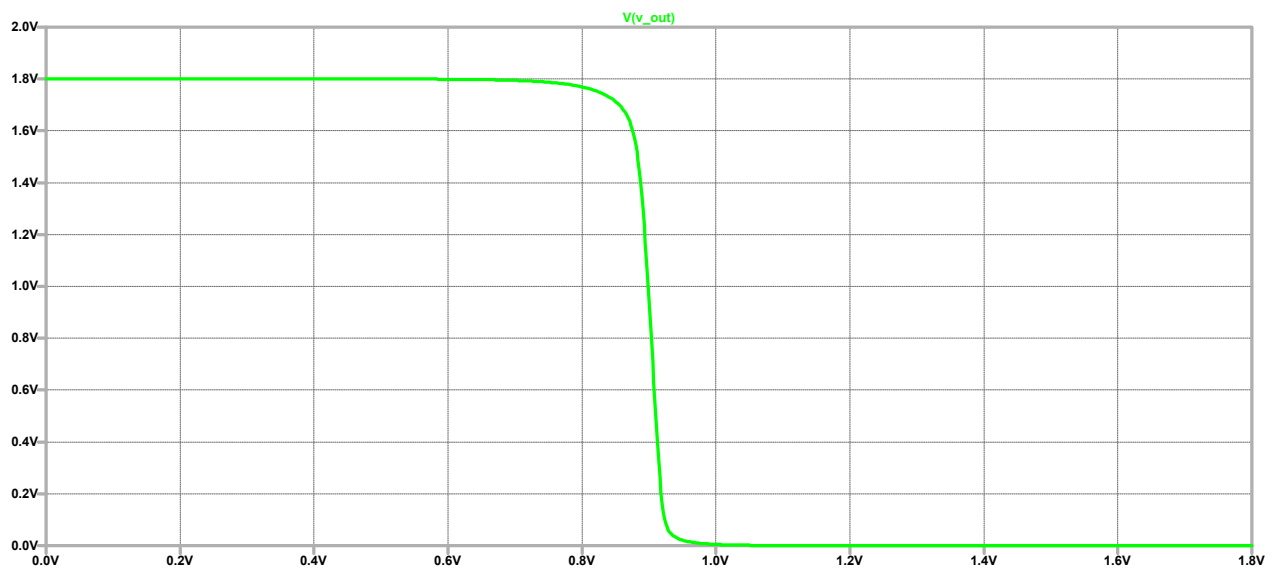


Figure 2: Inverter DC response

(b) Transient response,

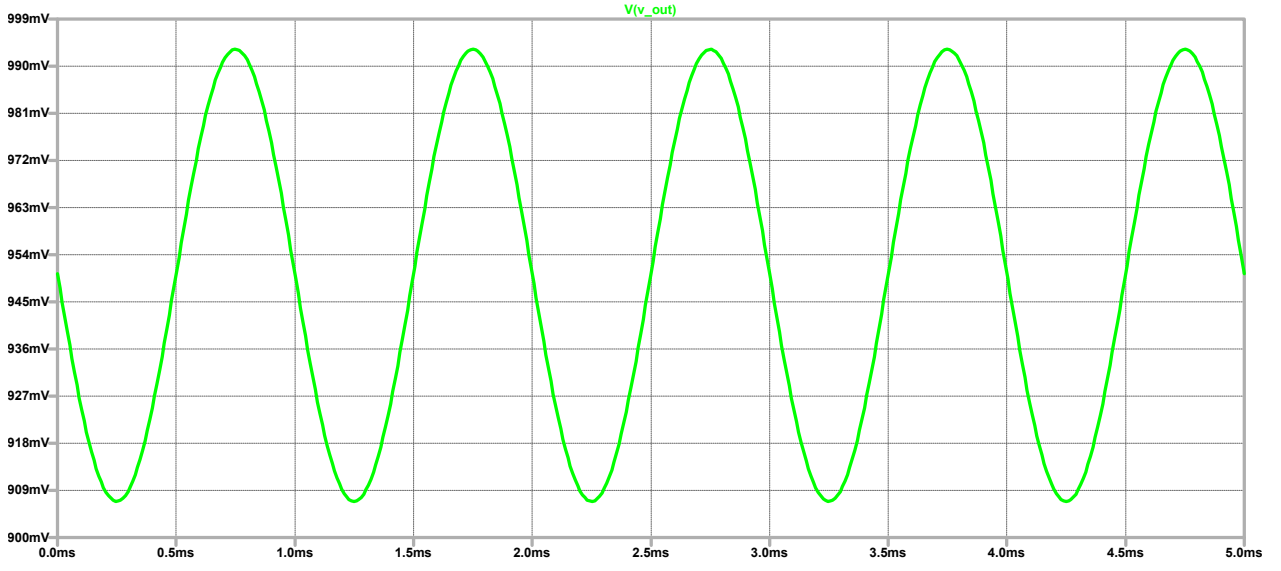


Figure 3: Inverter transient response

(c) AC response

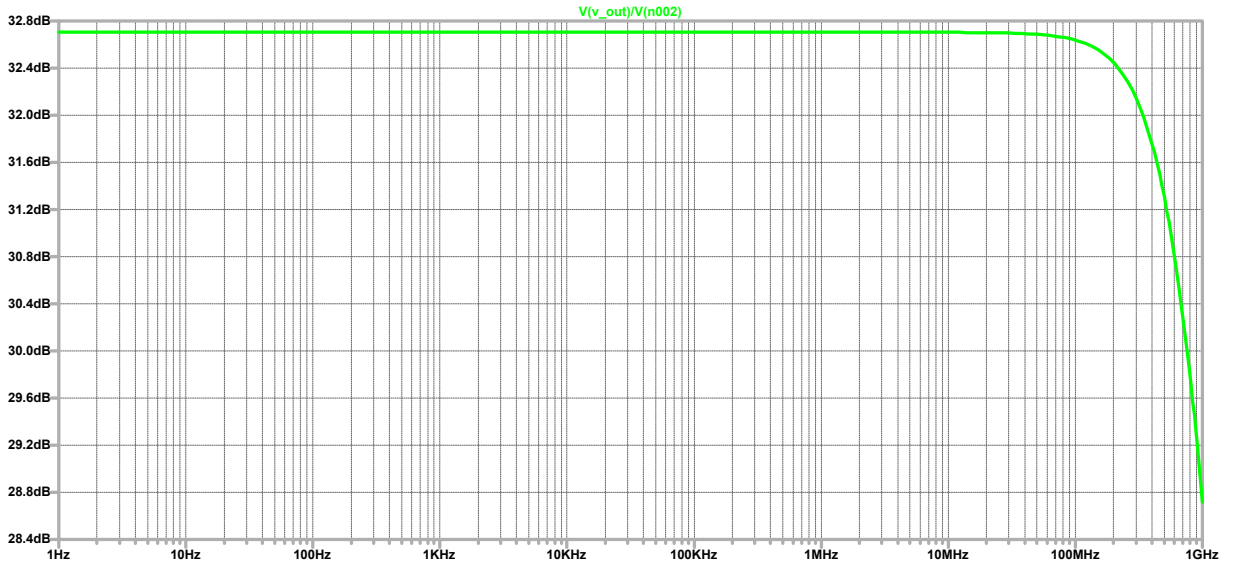


Figure 4: Inverter AC gain

$$\begin{aligned}
 \left| \frac{V_{out}}{V_{in}} \right| &= 32.7dB \\
 &= 43.2 \\
 \omega_p &= 2\pi f_{-3dB} \\
 &= 5.136 \times 10^9 \text{ rads}^{-1}
 \end{aligned}$$

(d) AC Response

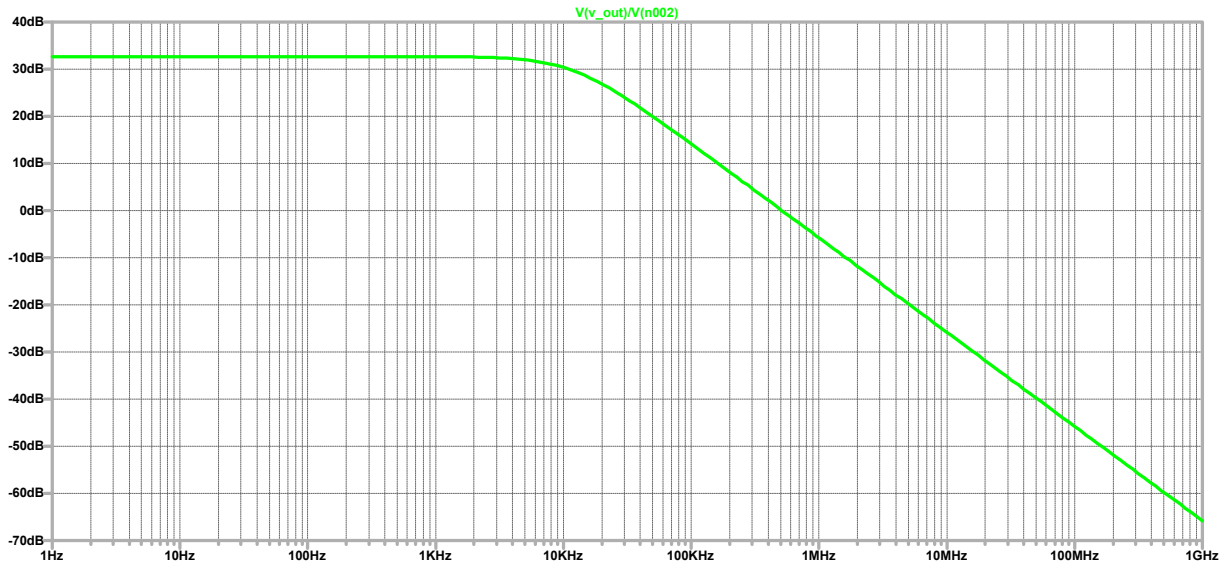


Figure 5: Inverter AC gain with output capacitor

$$\begin{aligned}
 \left| \frac{V_{out}}{V_{in}} \right| &= 32.7 \text{ dB} \\
 &= 43.2 \\
 \omega_p &= 2\pi f_{-3\text{dB}} \\
 &= 7.42 \times 10^4 \text{ rad/s}^{-1}
 \end{aligned}$$

(e) The pole at output node,

$$\begin{aligned}
 RC &= \frac{1}{2\pi f_c} \\
 R(C + \Delta C) &= \frac{1}{2\pi f_d} \\
 R &= \frac{1}{\Delta C} \left(\frac{1}{2\pi f_d} - \frac{1}{2\pi f_c} \right) \\
 &= \frac{1}{\Delta C} \left(\frac{1}{2\pi f_d} - \frac{1}{2\pi f_c} \right) \\
 R_{out} &= 134.75 \text{ k}\Omega
 \end{aligned}$$

Problem 4

(a) Testbench

```

.lib 'C:\Program Files\LTC\LTspiceXVII\lib\cmp\log018.l' TT
.dc V1 0 1.8 0.01
;ac dec 10 1 1G
;tran 0 5m 0 0.01 ;1 0 1.8

```

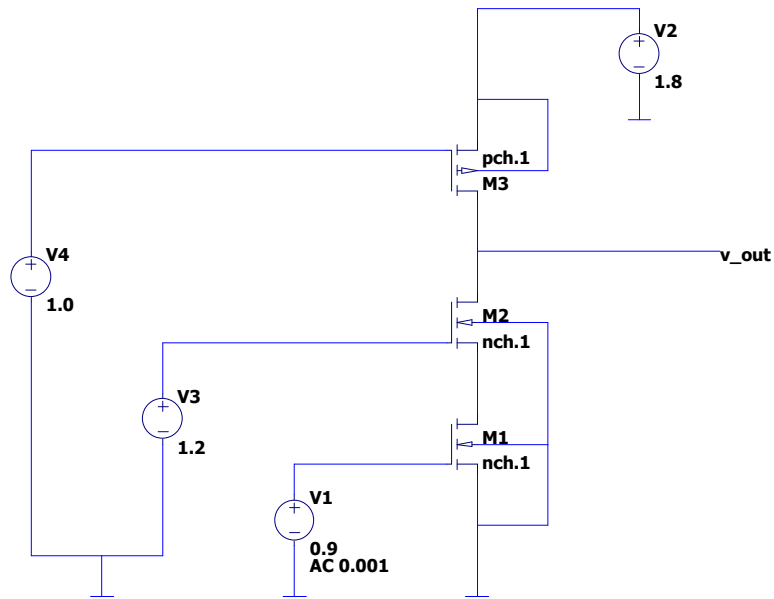


Figure 6: Testbench

DC transfer curve,

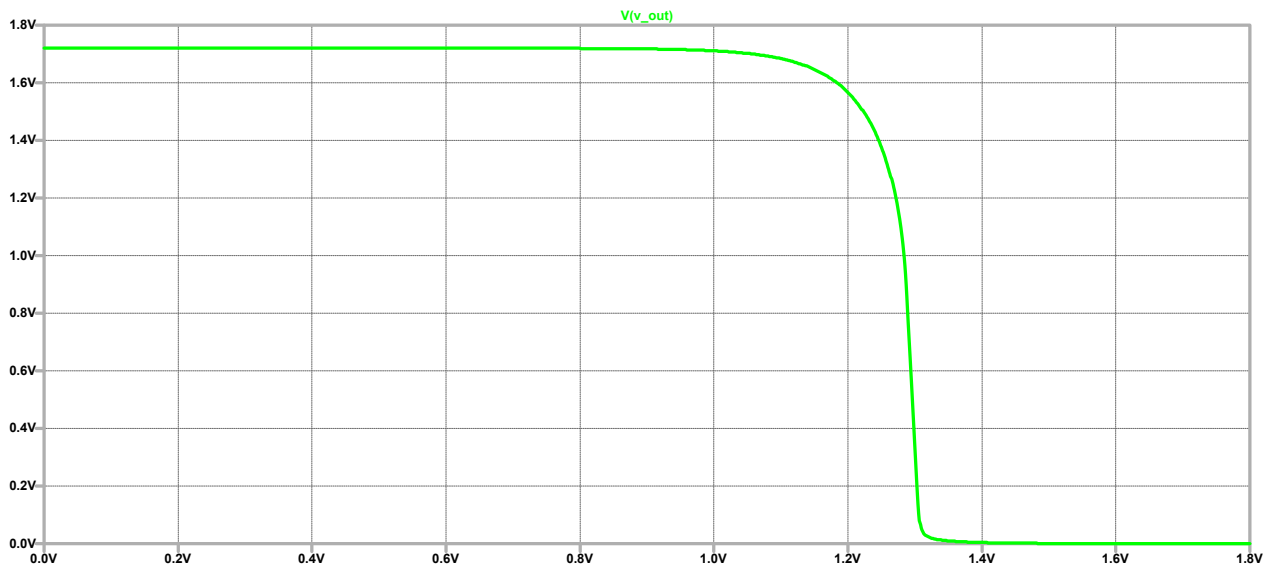


Figure 7: DC response

(b) Transient response,

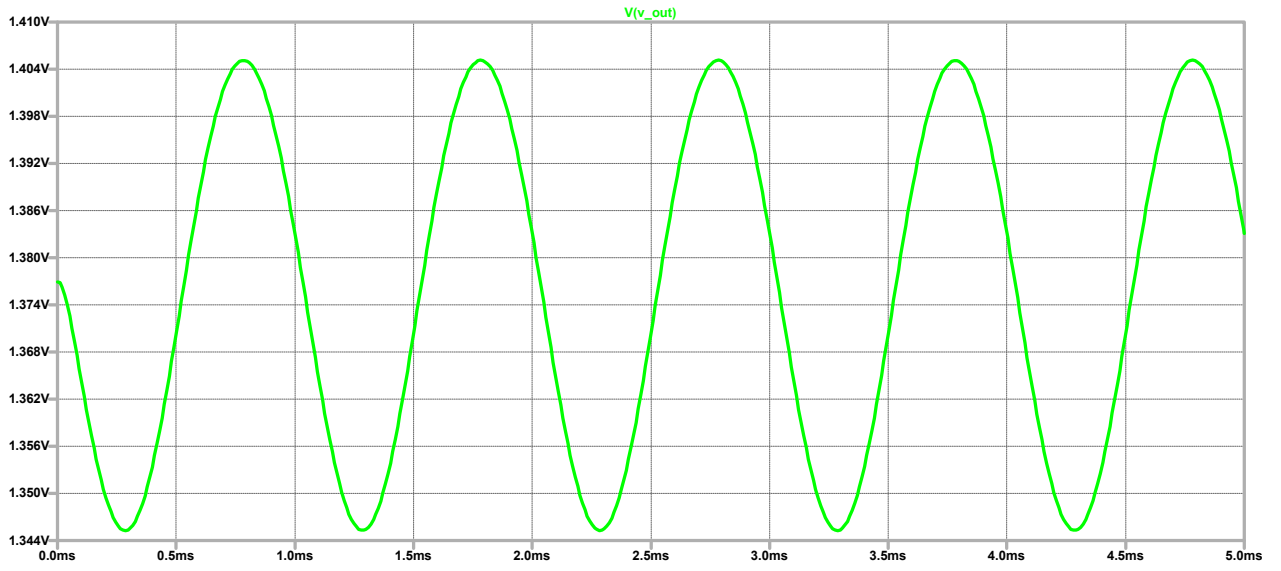


Figure 8: Transient response

(c) AC response

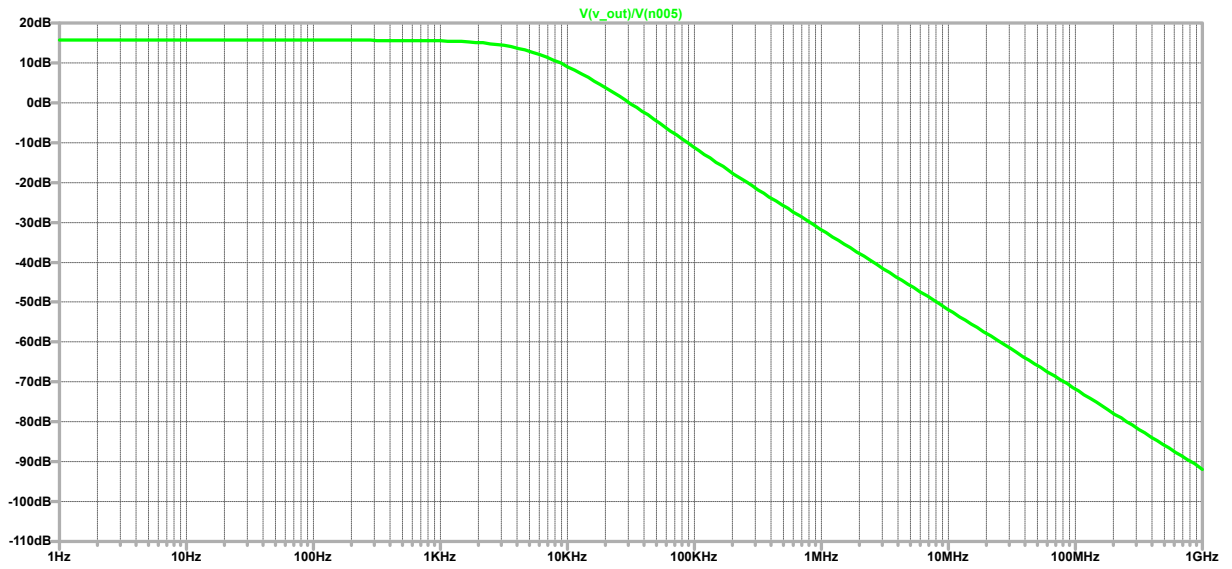


Figure 9: Inverter AC gain

$$\begin{aligned}
 \left| \frac{V_{out}}{V_{in}} \right| &= 15.7dB \\
 &= 6.06 \\
 \omega_p &= 2\pi f_{-3dB} \\
 &= 3.35 \times 10^4 \text{ rad/s}^{-1}
 \end{aligned}$$

(d) Gain bandwidth product, GBWP

$$\begin{aligned}
 \left| \frac{V_{out}}{V_{in}} \right| &= 6.06 \\
 f_{-3dB} &= 5.331 \text{ kHz} \\
 GBWP &= 32.3 \text{ kHz}
 \end{aligned}$$